

SYNTHESIS REPORT

P.V.S.L Hari Chandana 16CS30026

P. Anusha 16CS30027

Speed of operation:

Booth multiplier:

Minimum period: 2.067ns (Maximum Frequency: 483.887MHz)

Minimum input arrival time before clock: 1.781ns

Maximum output required time after clock: 0.673ns

Maximum combinational path delay: No path found

Combinational multiplier:

Maximum combinational path delay: 13.183ns

Array multiplier:

Maximum combinational path delay: 10.292ns

Hardware requirement:

Booth multiplier:

# Adders/Subtractors	: 2
6-bit adder	: 1
6-bit subtractor	: 1
# Counters	: 1
3-bit up counter	: 1
# Registers	: 14
Flip-Flops	: 14
# Comparators	: 1
3-bit comparator greater	: 1
# Multiplexers	: 5
6-bit 2-to-1 multiplexer	: 2
7-bit 2-to-1 multiplexer	: 3

Combinational multiplier:

# Adders/Subtractors	: 59
16-bit subtractor	: 1
2-bit adder	: 8
2-bit adder carry in	: 48
8-bit subtractor	: 2
# Multiplexers	: 3
16-bit 2-to-1 multiplexer	: 1
8-bit 2-to-1 multiplexer	: 2
# Xors	: 1
1-bit xor2	: 1

Array Multiplier:

# Adders/Subtractors	: 56
2-bit adder	: 8
2-bit adder carry in	: 48

Conclusion: The speed of booth-multiplier is very less as compared to the other two also the hardware required by the booth multiplier is very much optimized. Array multiplier requires a lot of hardware and it will become very tedious to implement larger multiplications.